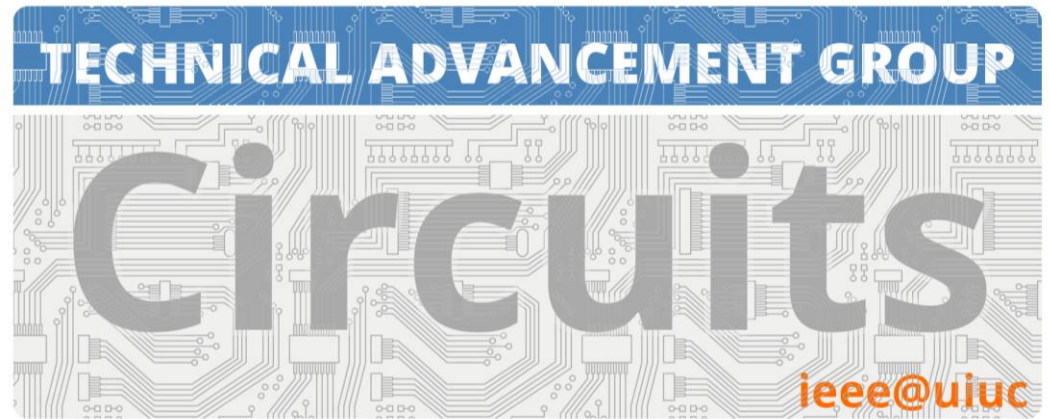


Bass Boost Amp Workshop Overview

Brady Salz
November 16, 2015




HIGH LEVEL


- Component Overview
- Ideal Amp
- Gain $\leftrightarrow$ Bandwidth Tradeoffs
- Implementation
- PCB
- Sources

OP AMPS

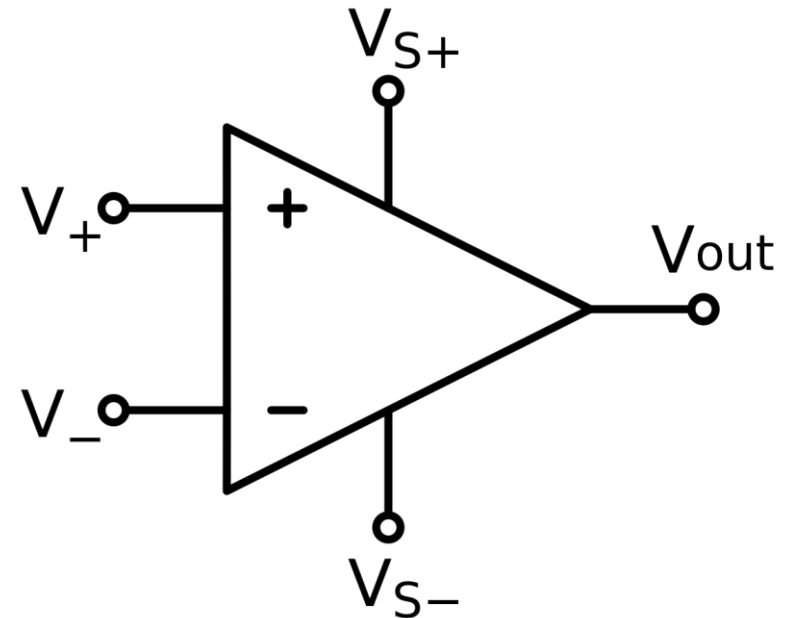- **5 Terminal Device!**
 - Positive/Negative INPUT
 - Positive/Negative SUPPLY
 - OUTPUT
 - Tend to not draw the supply
- **Complex to make**
 - 15+ transistors usually
- **Op amps have 2 “Golden Rules”**
 - No current flows INTO the INPUTS
 - The output does whatever it has to in order to make the positive input equal the negative input




BLOCK DIAGRAM

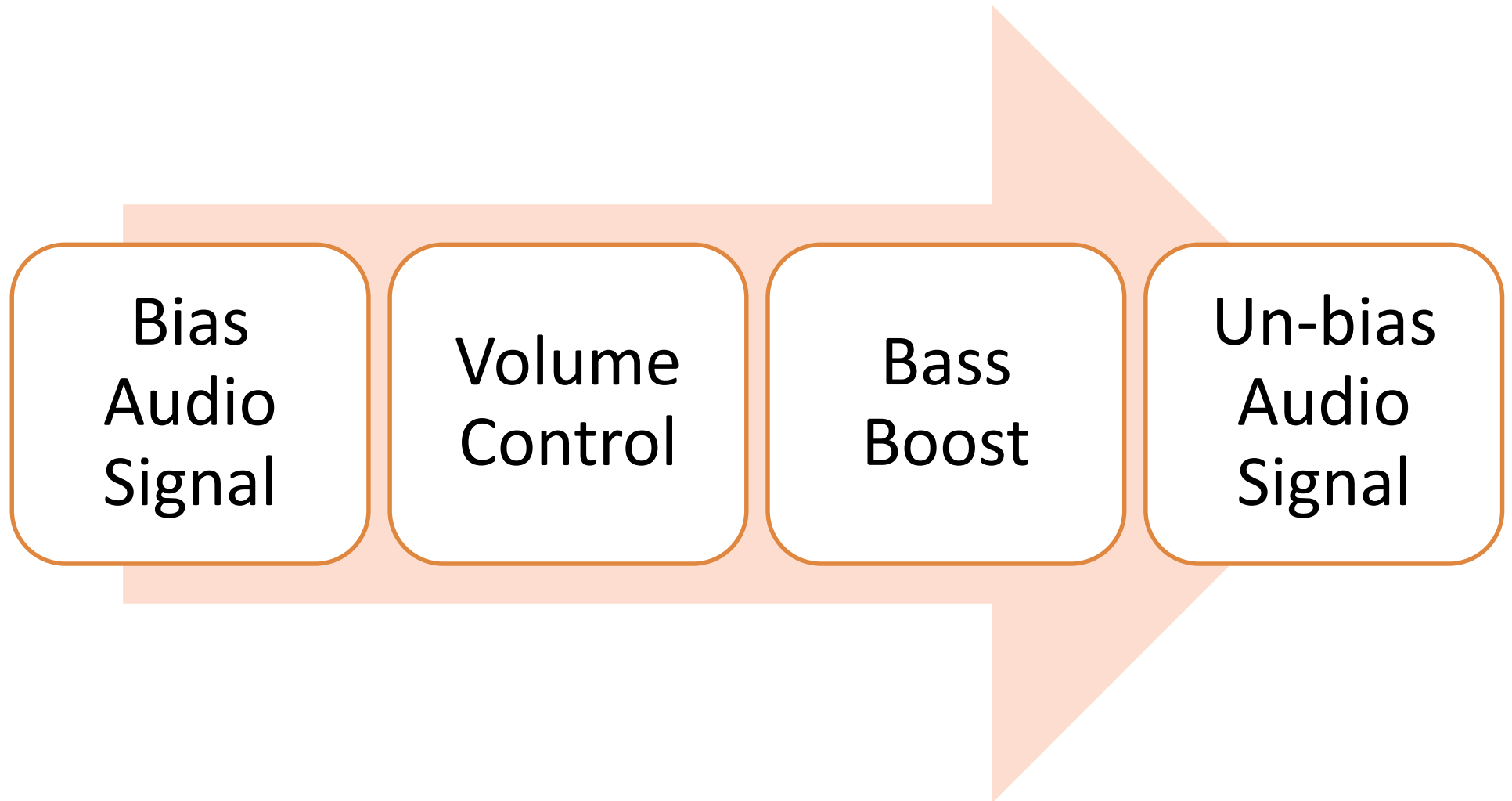


BIASING

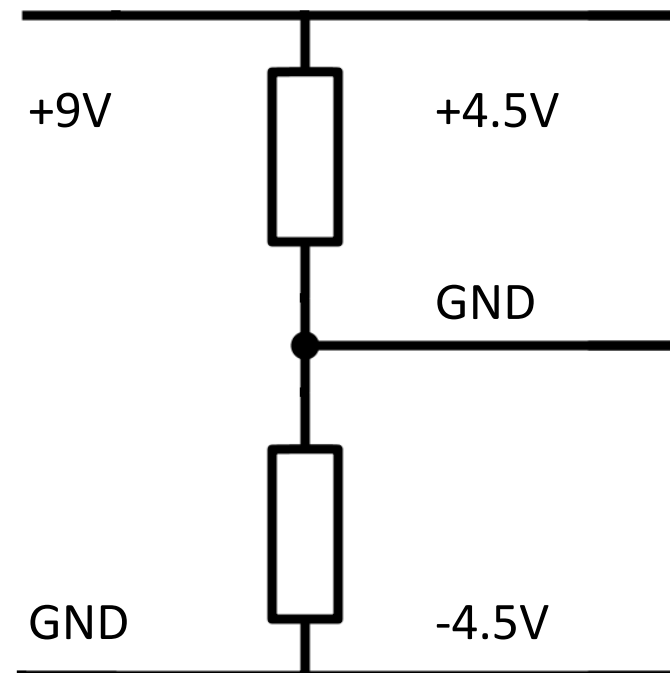- Audio signals are 0V centered (+/- 0.450mV approximately)
 - But we only have one 9V battery to power this!
- Need a rail splitter!
- Creates a *virtual ground* for us to use
- Not a “real” ground, still moves up and down slightly



VOLUME CONTROL

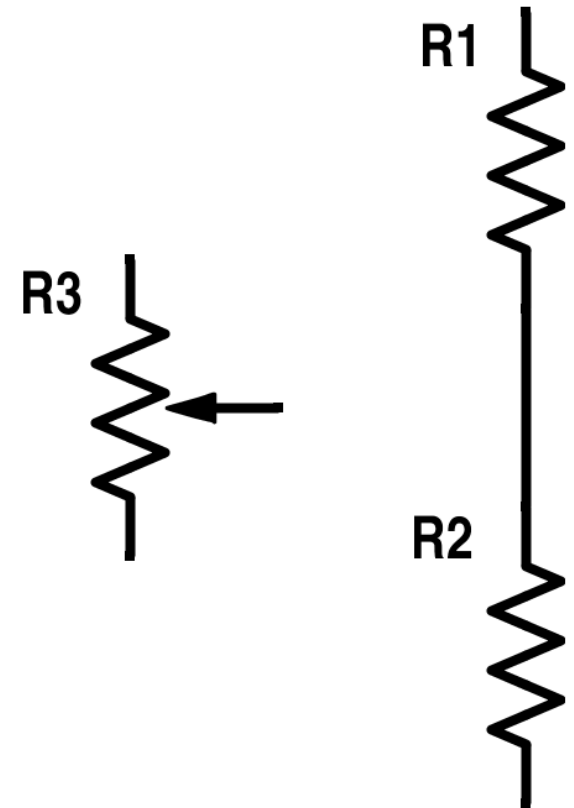- Humans hear in dB (logarithmically)
 - 2x interpreted volume means a 10x change in amplitude
- Need a circuit that change an input wave logarithmically
- Use a log potentiometer
- Gain is $\frac{R_2}{R_2 + R_1}$
 - Always less than one!



GAIN


- Simple op amp circuit
- Non inverting amplifier

Can solve using KCL!

$$\frac{V_{out} - V_-}{R_2} = \frac{V_- - 0}{R_1}$$

$$V_- = V_{in}$$
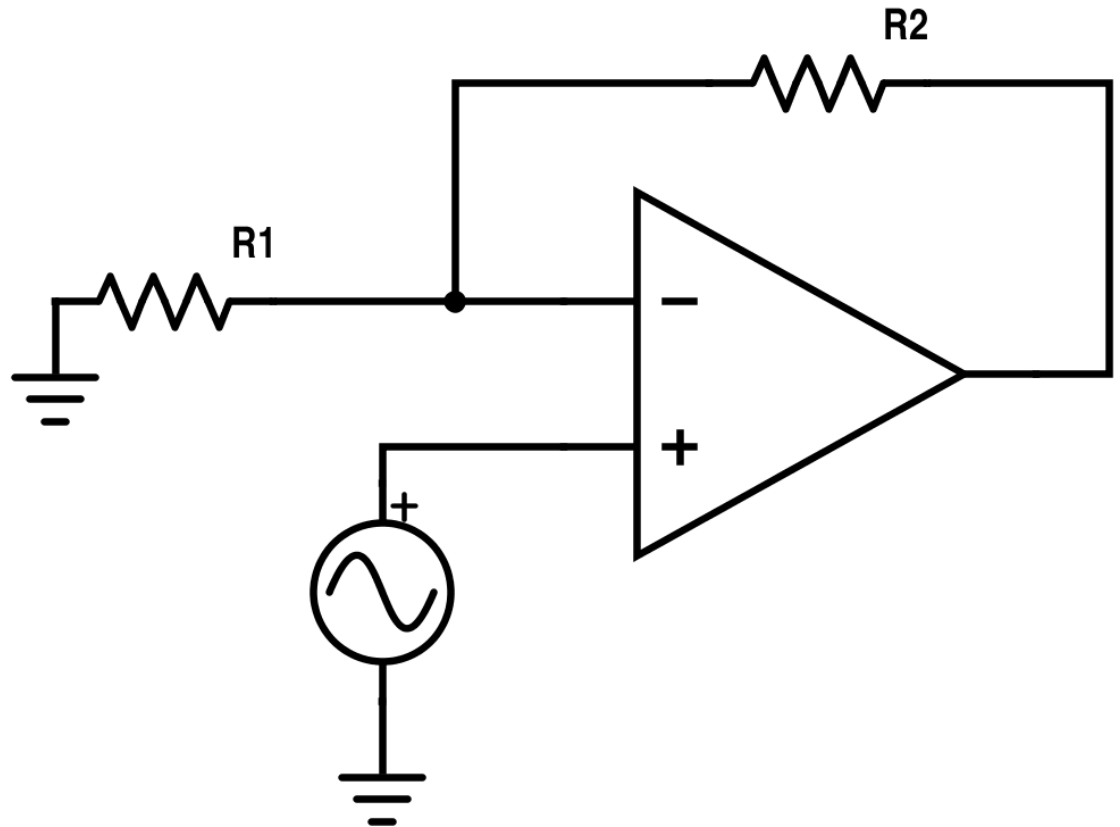
$$V_{out} = \left(1 + \frac{R_2}{R_1}\right) V_{in}$$




LOW PASS FILTER

- Need an element that has a different response at low + high frequencies
- Solve with a parallel RC circuit



Impedance of circuit is :

$$Z_{RC} = R || \frac{1}{j\omega C} = \frac{1}{\frac{1}{R} + j\omega C} = \frac{R}{1 + j\omega RC}$$

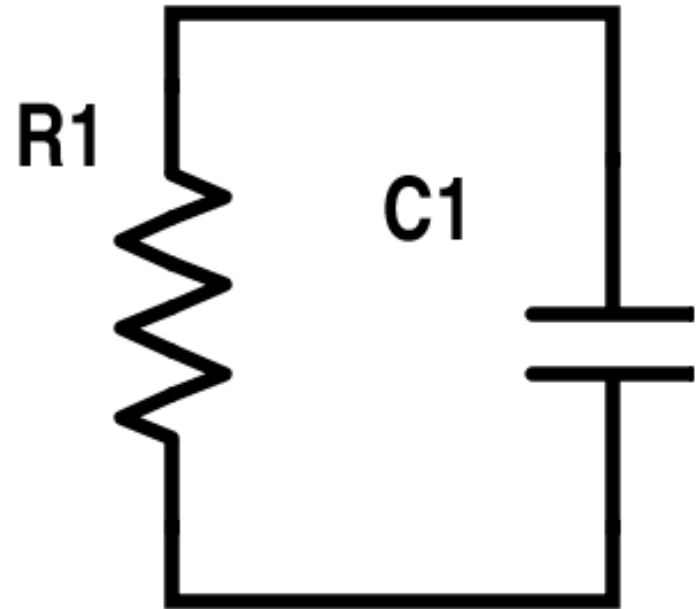

LOW PASS FILTER

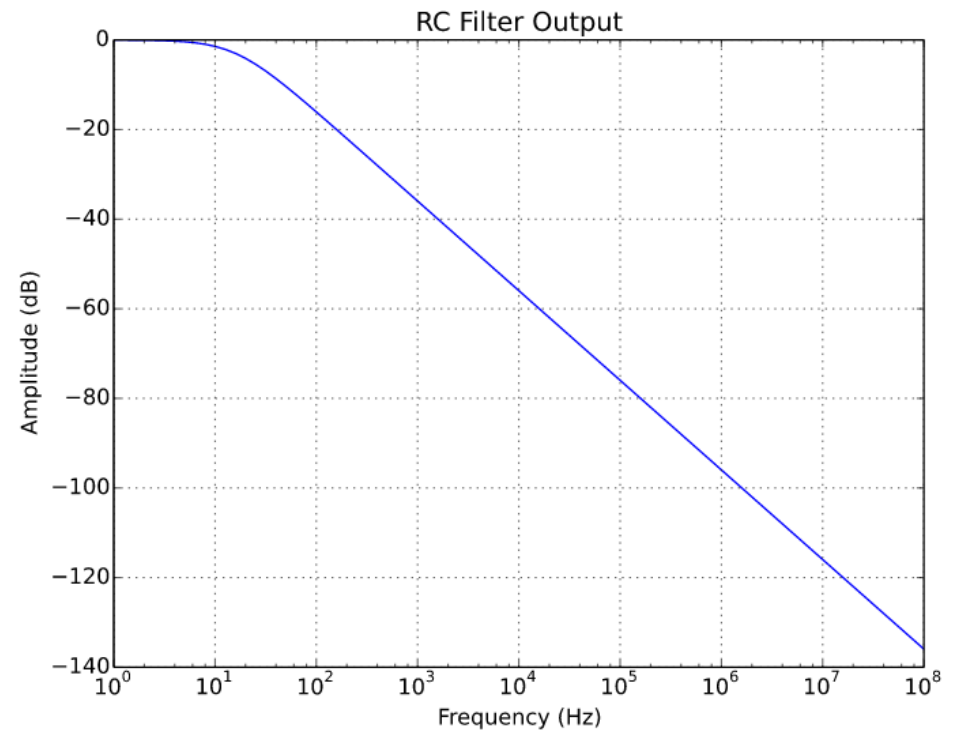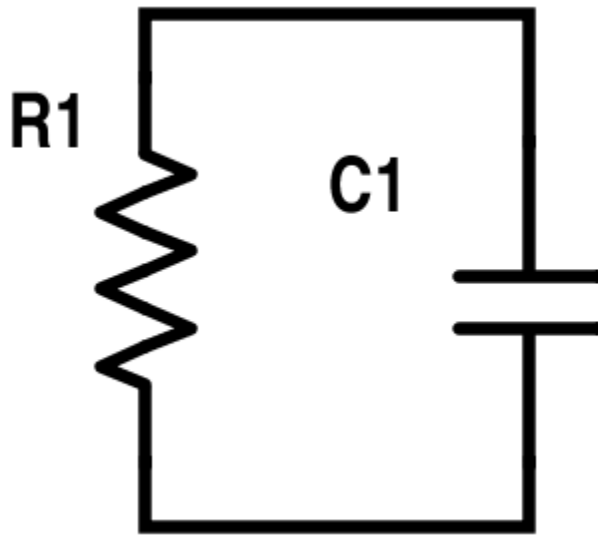
- See R at low frequencies, decreasing as ω increases
- Can view as a filtering element!



BASS BOOST

- Now let's combine the last two ideas!
- We now have an amplifier with variable gain based on the frequency!
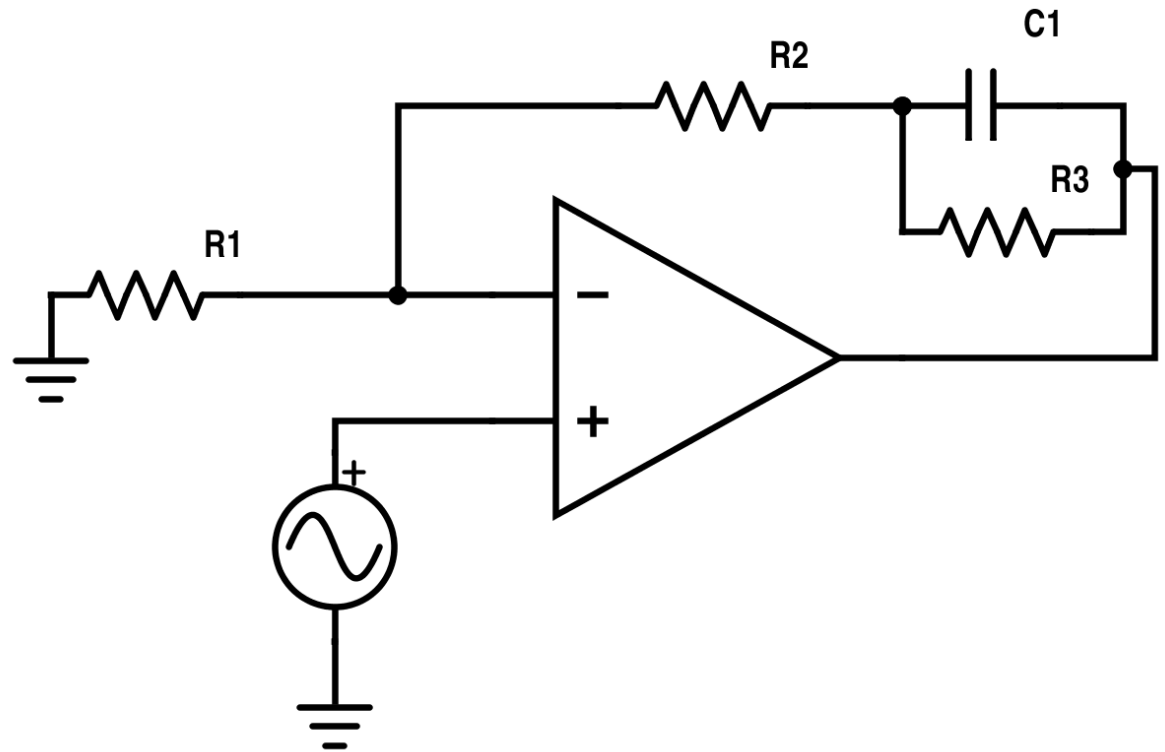
$$V_{out} = \left(1 + \frac{R_2 + Z_{RC}}{R_1} \right) V_{in}$$



GAIN BANDWIDTH

- Have a tuning knob to change that resistor, but...
- Nothing in life is free!
- If we want to boost more bass, we get less boost
- If we want to have stronger boost, we boost less bass

WHY

GAIN BANDWIDTH

- Gain is proportional to resistance
 - More gain, higher R

$$V_{out} = \left(1 + \frac{R_2 + Z_{RC}}{R_1} \right) V_{in}$$


- Bandwidth is inverse to resistance
 - More frequencies, lower R

$$Z_{RC} = \frac{R}{1 + j\omega RC}$$

- Relationship called Gain-Bandwidth Product (can prove with integrals)

INPUT SIDE

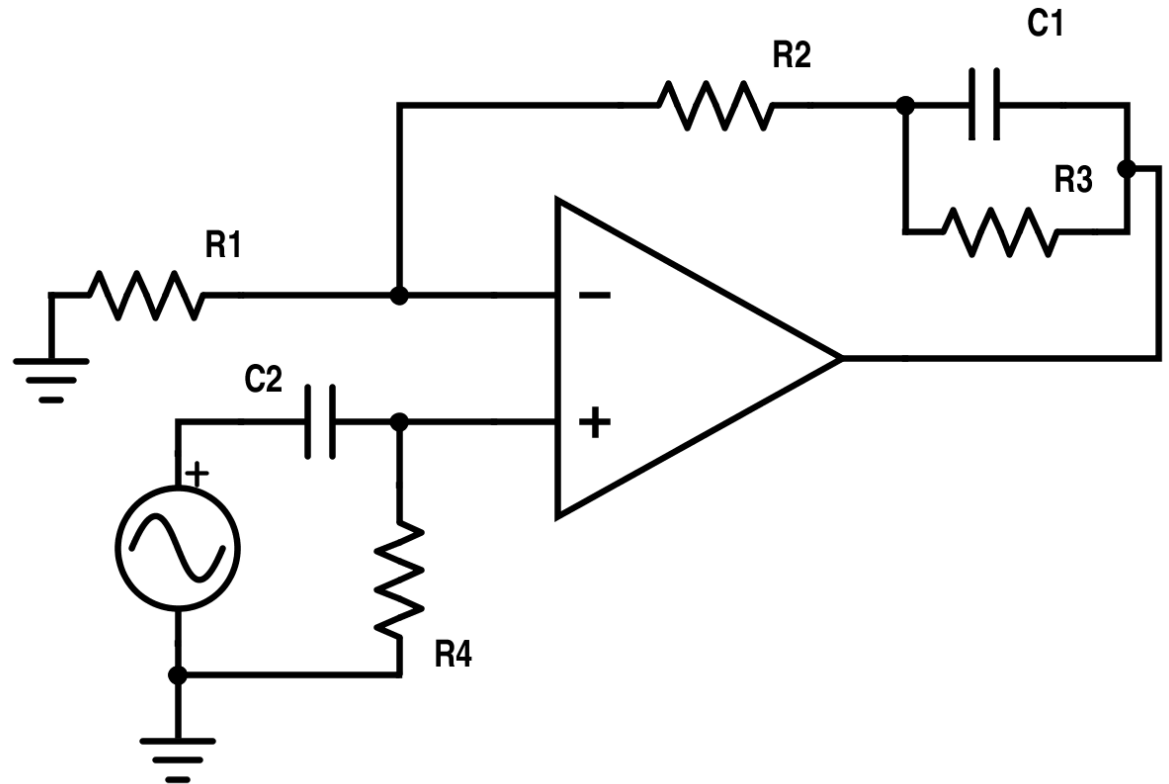- High pass filter into op amp
- Don't want any DC going to the output/headphones
- Opposite of parallel RC
- Has “rising” effect with frequency
 - Blocks low frequencies
 - Leaves high frequencies alone
 - Choose cutoff as 2-5 Hz



ADVANCED – INPUT BIAS


- Ideally, op amp inputs are the same voltage
- Not always that lucky, often get a term called “input bias” or “offset voltage”
- Shows up as a linear distortion term

$$V_{out} = \left(1 + \frac{R_2 + Z_{RC}}{R_1} \right) (V_{in} + V_{OS})$$

Our op amp has maximum offset voltage of 75uV – not bad!


ADVANCED - NOISE

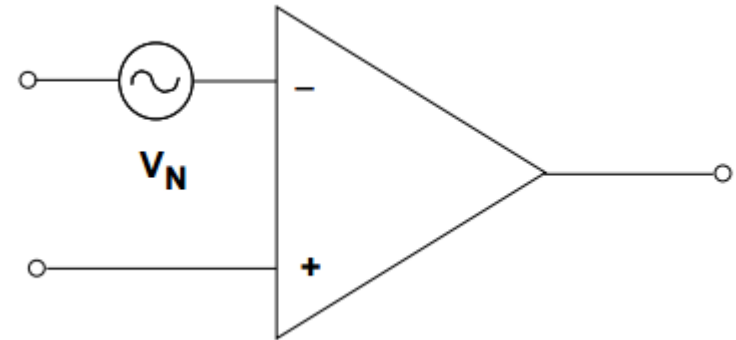- Every amplifier has some noise input
- Get noise across all frequencies!
- Define noise as $V/\sqrt{\text{Hz}}$ (voltage per square root Hertz)
- Plug in bandwidth of circuit -> get noise power
- Ours has $3\text{nV}/\sqrt{\text{Hz}}$ -> $3\text{nV}/\sqrt{\text{Hz}} * \sqrt{20\text{kHz}} = 0.42\mu\text{V}_{\text{rms}}$



ADVANCED - PSRR

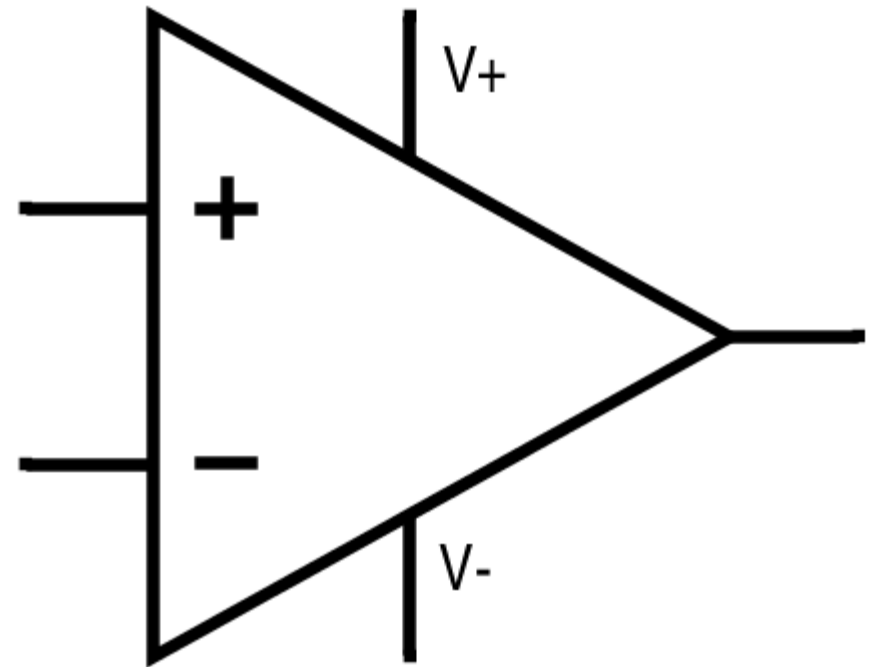- Op amps don't have three terminals, they have FIVE
- If the supply voltage changes, how much should the output change?
- Ideally none, but of course it's dependent
- Called "Power Supply Rejection Ratio" – PSRR
- Ours has $0.5\mu\text{V}/\text{V}$ (output/supply)



SWITCHES


- All switches can be characterized into types

- MBB (Make Before Break)
- BBM (Break Before Make)


- Which one is better?

- Depends on application

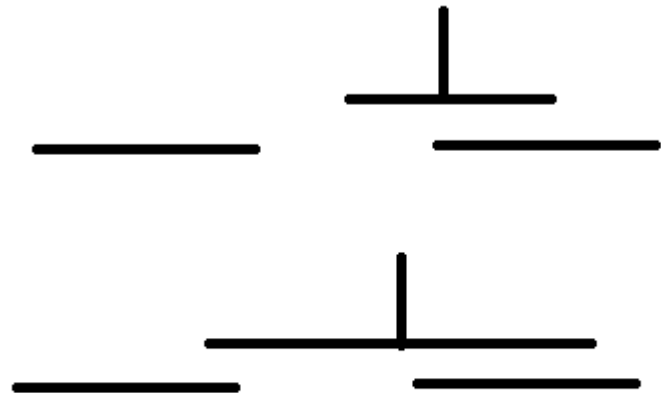
- For this circuit, we use BBM to prevent short circuits



SCHEMATIC

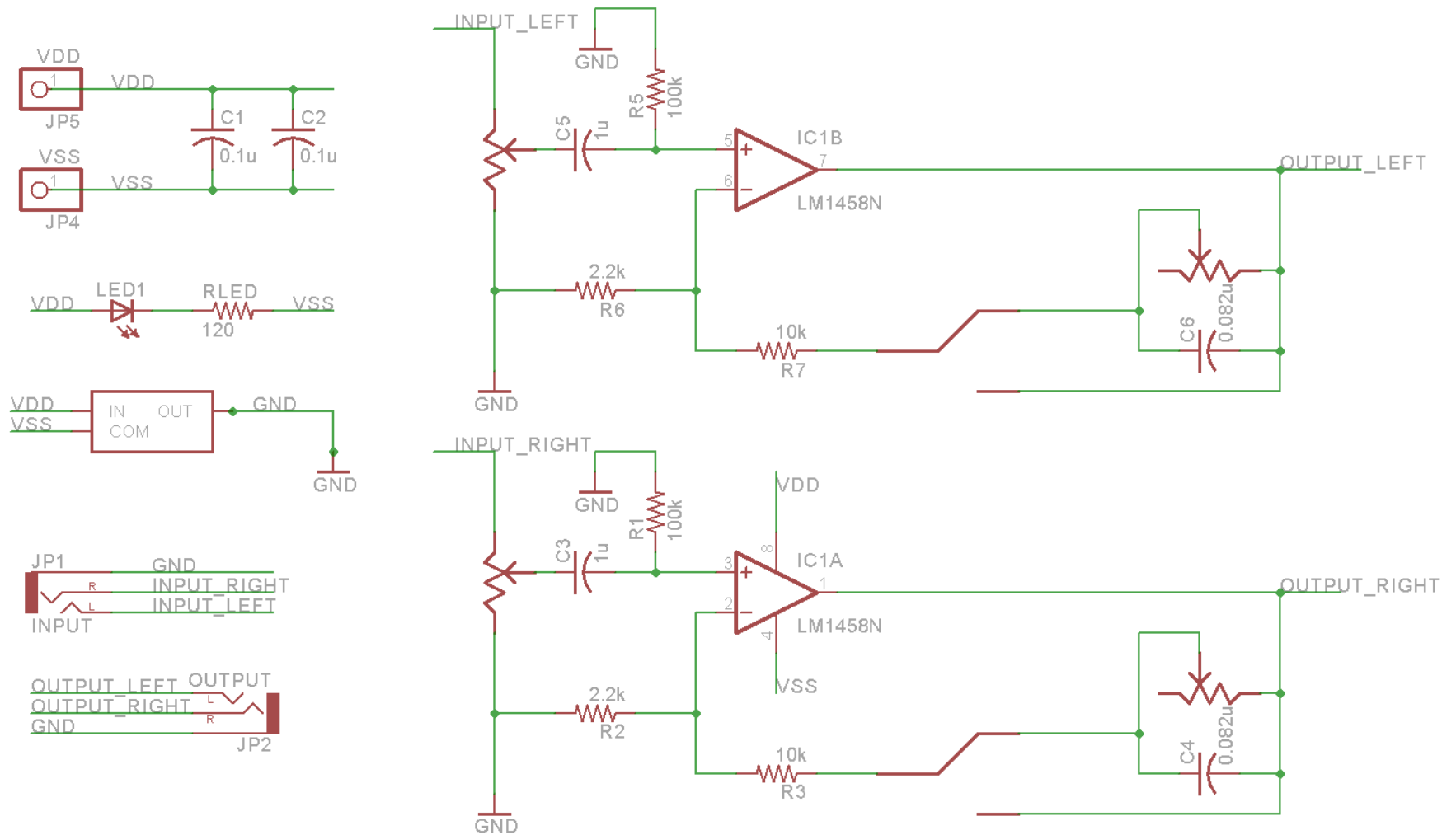

BOARD

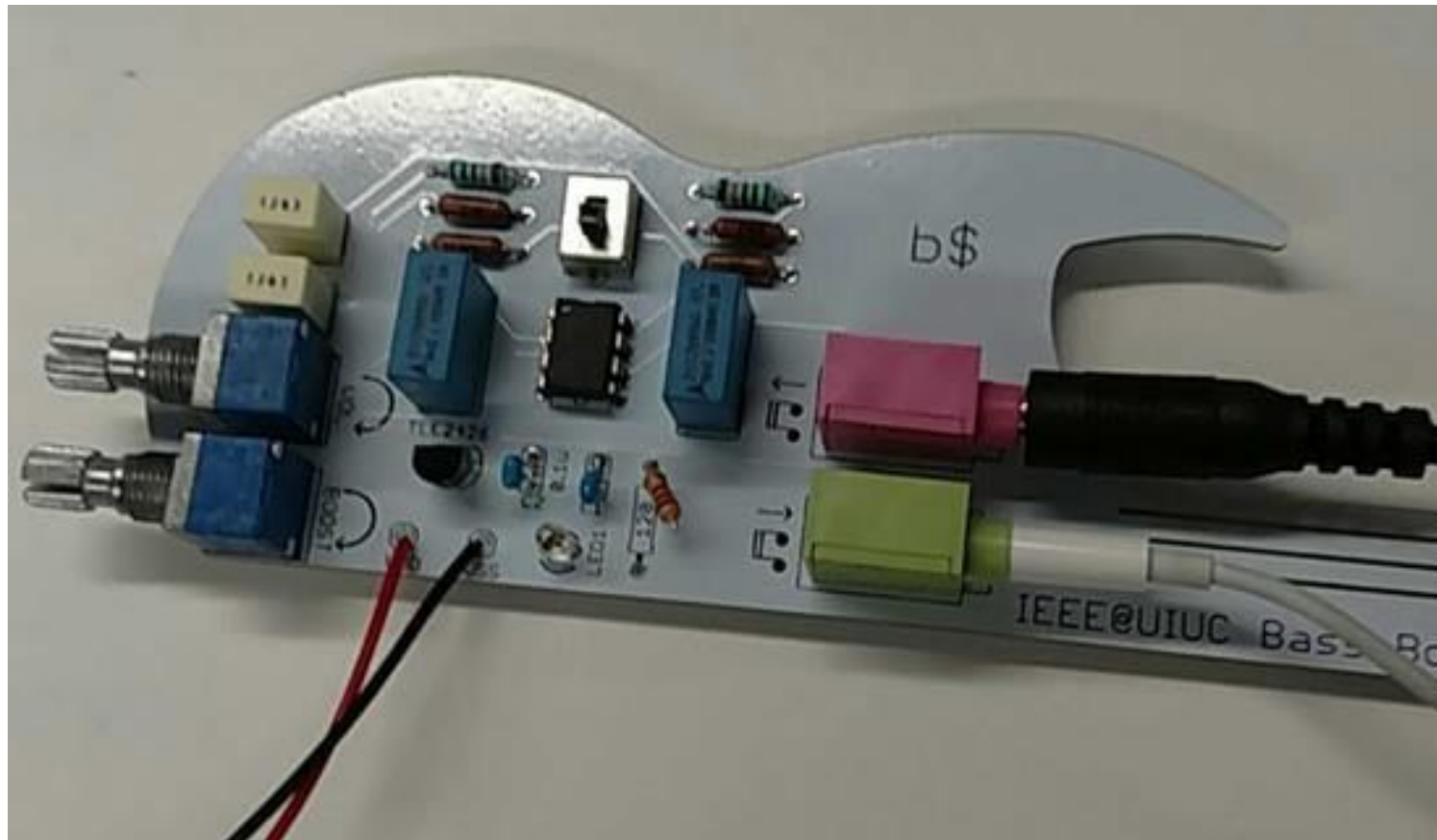

CITATIONS

- “CMoy Pocket Amplifier” by Warren Young
<http://tangentsoft.net/audio/cmoy/>
- OPA2227 Datasheet
<http://www.ti.com/lit/ds/symlink/opa2227.pdf>
- “Op Amp Noise” – Analog Devices
<http://www.analog.com/media/en/training-seminars/tutorials/MT-047.pdf>
- “Op Amps for Everyone” – Ron Mancini
http://123.physics.ucdavis.edu/week_1_files/opamps.pdf

HOW TO USE

- Turn volume, boost to ZERO (CCW)
- Maximize input source volume (laptop, phone, etc)
- Slowly turn up volume to acceptable level
- Slowly turn boost to acceptable level
 - If not apparent, hit the switch
- ENJOY
- P.S. It's a preamp, not an amp!

