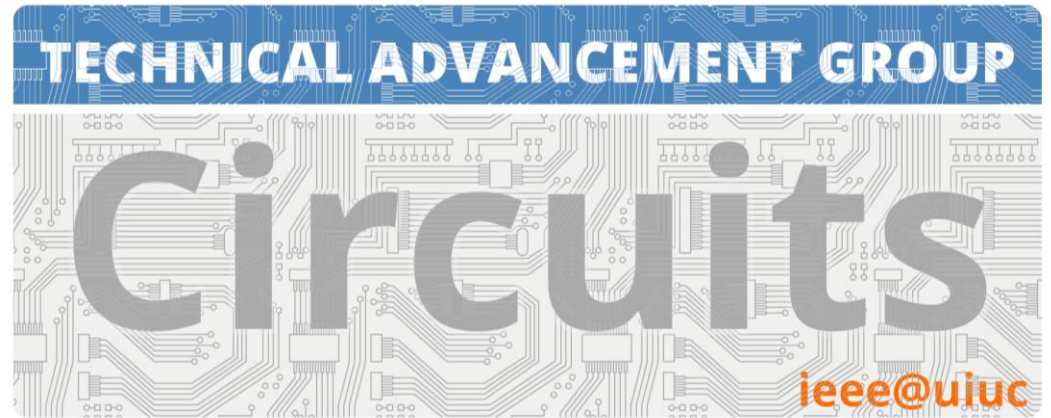


# Boost Converter Workshop Overview

Brady Salz  
October 11, 2015



# HIGH LEVEL

- Component Overview
- Ideal Converter
- Real Converter
- Implementation
- PCB


# INDUCTOR

- $E = LI$  or  $V = L di/dt$  or  $Z = j\omega L$
- AC "blocks", DC "shorts"
- "Opposite" of a capacitor
- Easy to make, hard to make precise
- Often used in RF or Oscillator circuits for tuning



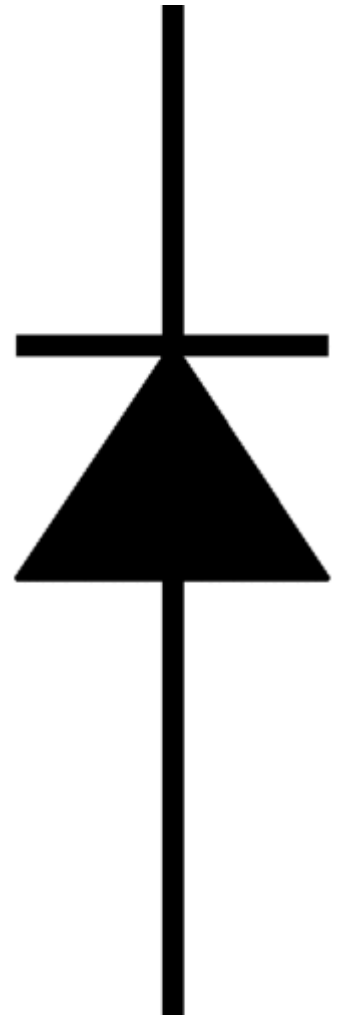
# DIODE

- Exponential IV curve
  - Can linearize to  $V > V_d$ , unlimited current,  $V < V_d$ ,
- Negative/Low voltage “block”, else “short”
- Used for rectifiers, reverse polarity, voltage regulator
- Orientation matters!!
  - Does not behave the same both ways



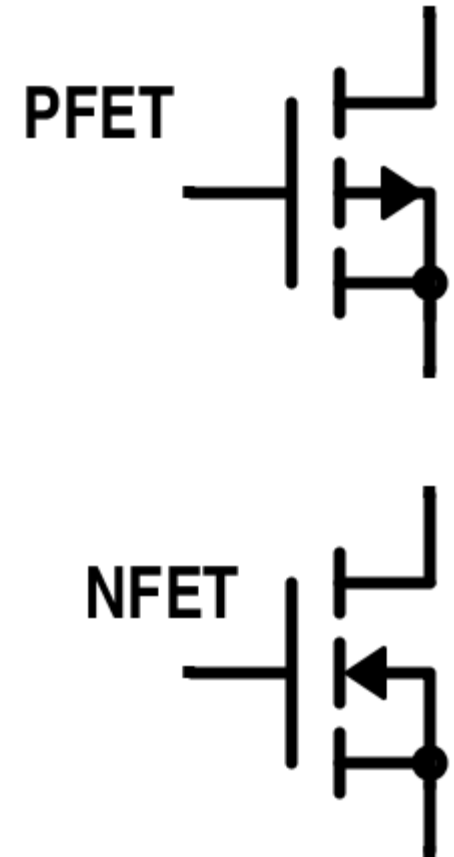
# MOSFET (PFET/NFET)

- Voltage-Controlled Current Source
- 3 Terminals – Drain Gate Source
- Two ways of viewing it (nFET):
  - Binary
    - Low voltage at gate, close up D-S connection (no current)
    - High voltage at gate, open up D-S connection (current)
  - Continuous
    - Current through D-S is proportional to gate voltage
    - Has a min/max (off/saturated) point
- pFET – same rules, just flip high flow (no current when high @ gate, etc)




# IDEAL SCHEMATIC

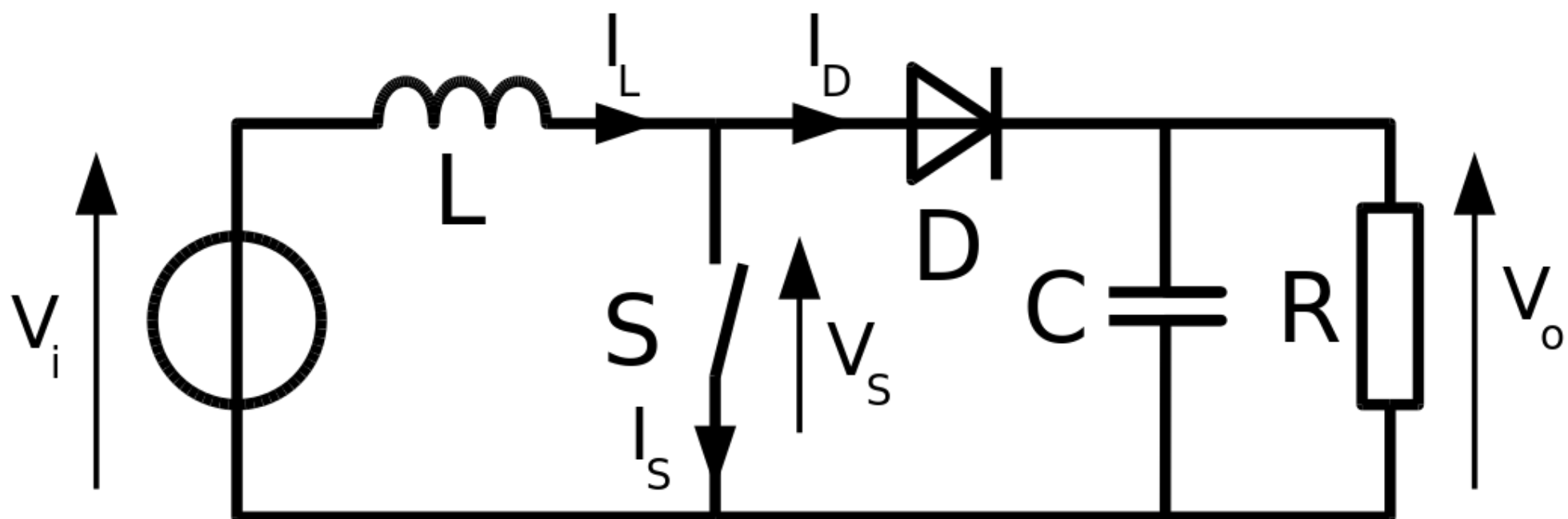


# TWO STATES

ON STATE

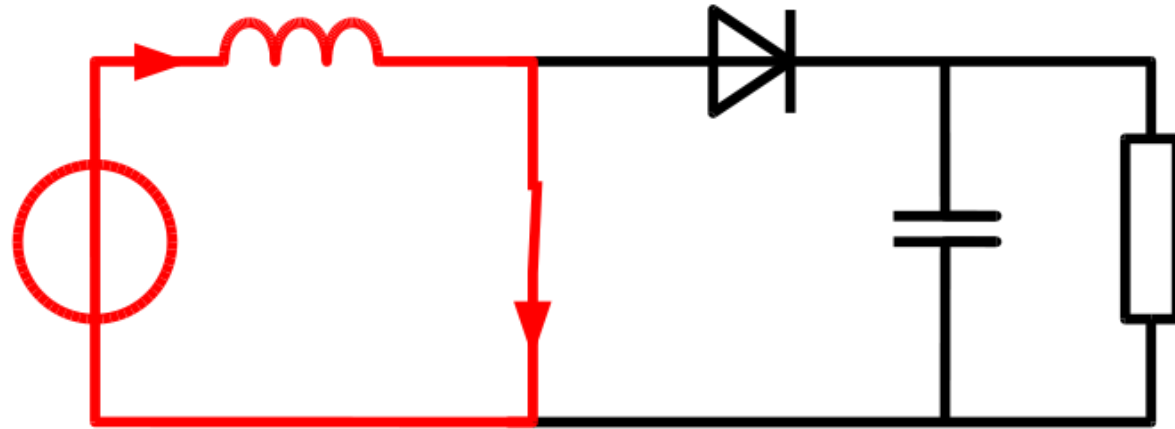

OFF STATE

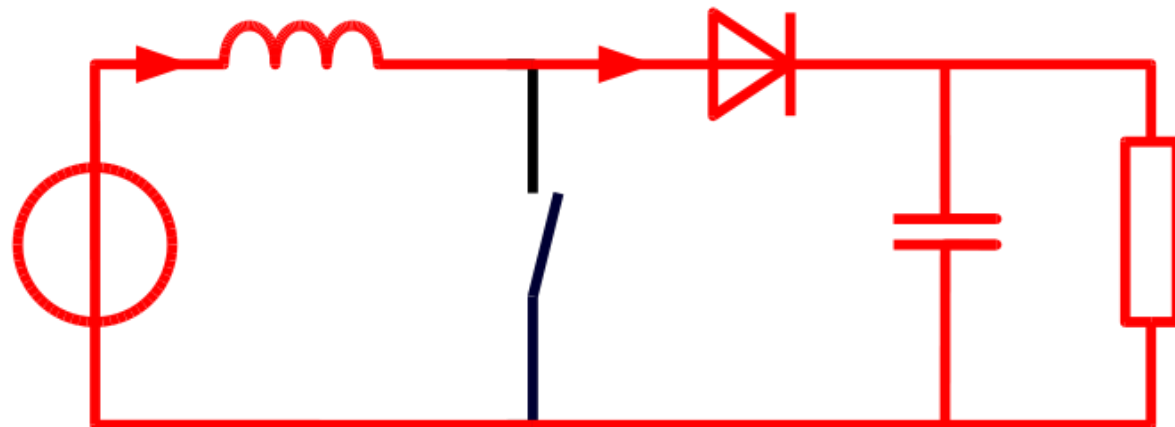

# DERIVATION

This “should be” a DC circuit with constant output voltage


- > Implies DC current as well
- > DC current means no inductor voltage

Assume driving switch with square wave


$$\begin{aligned}V_{L,\text{on}} + V_{L,\text{off}} &= 0 \\T_{\text{on}}V_{\text{in}} + T_{\text{off}}(V_{\text{in}} - V_{\text{out}}) &= 0 \\T_{\text{period}}(DV_{\text{in}} + (1 - D)(V_{\text{in}} - V_{\text{out}})) &= 0 \\DV_{\text{in}} + V_{\text{in}} - V_{\text{out}} - DV_{\text{in}} + DV_{\text{out}} &= 0 \\V_{\text{in}} - (1 - D)V_{\text{out}} &= 0 \\V_{\text{in}} &= (1 - D)V_{\text{out}} \\V_{\text{out}} &= V_{\text{in}} / (1 - D)\end{aligned}$$




# WAVEFORMS

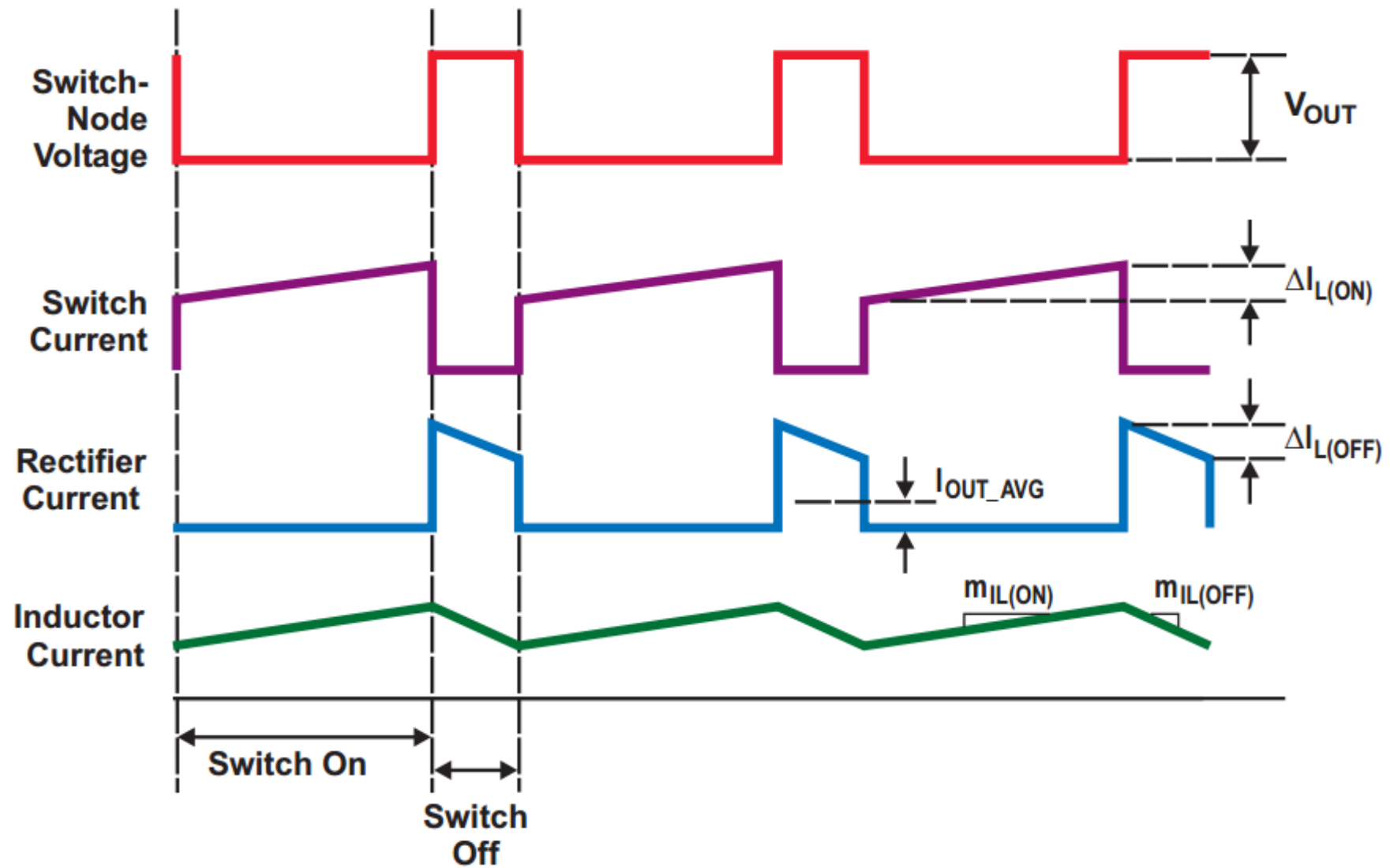


# BASIC NON-IDEALITIES

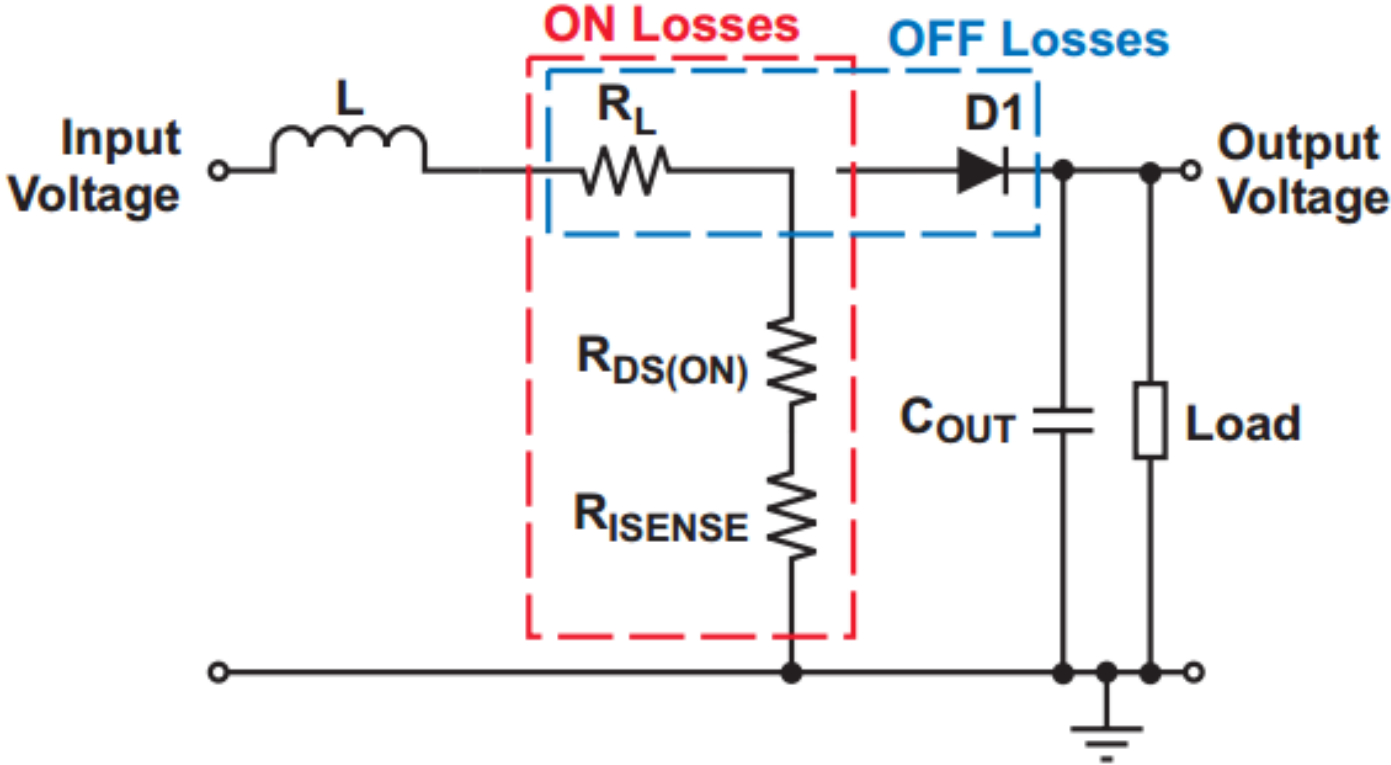

# MORE NON-IDEALITIES

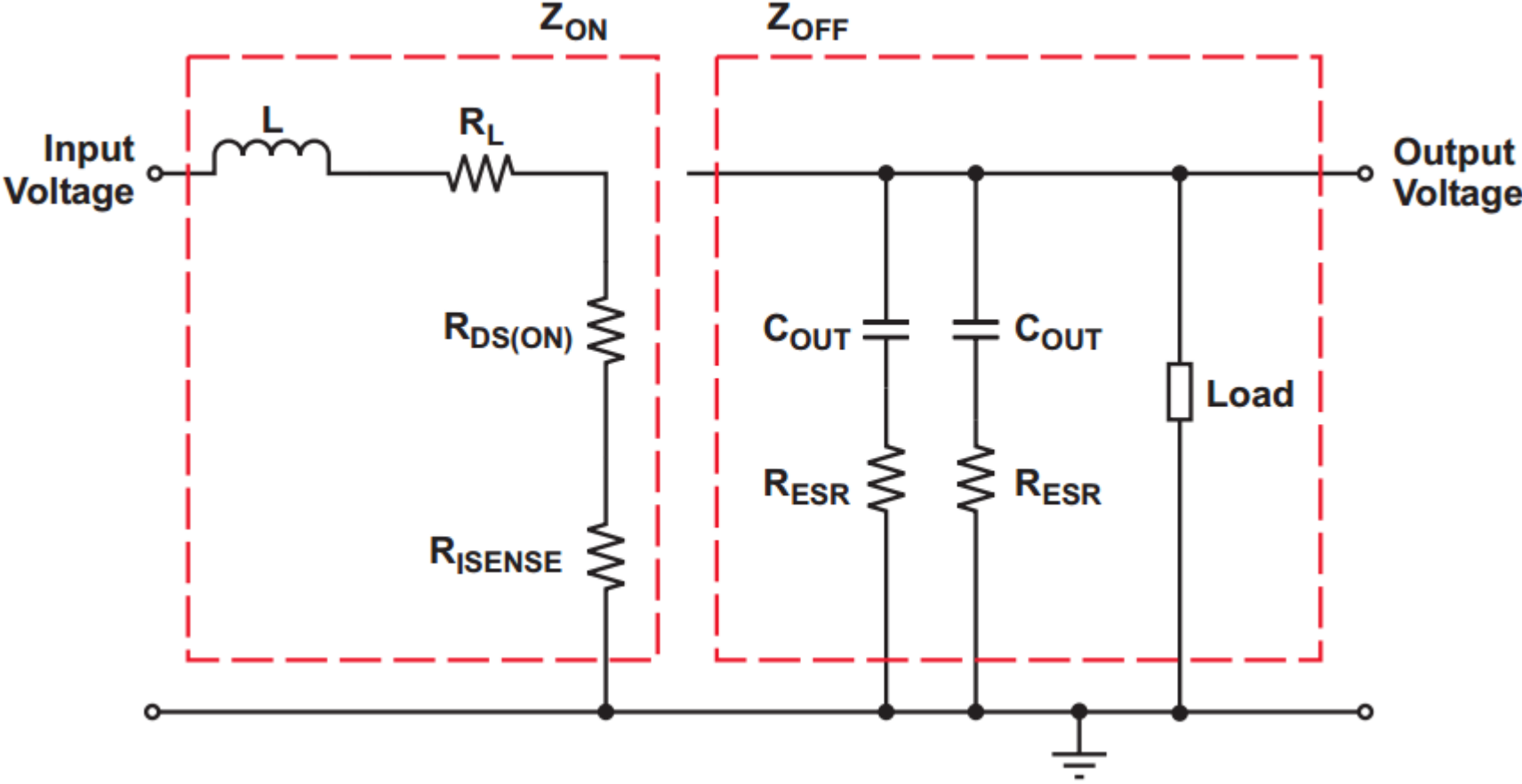


# FOURIER SERIES

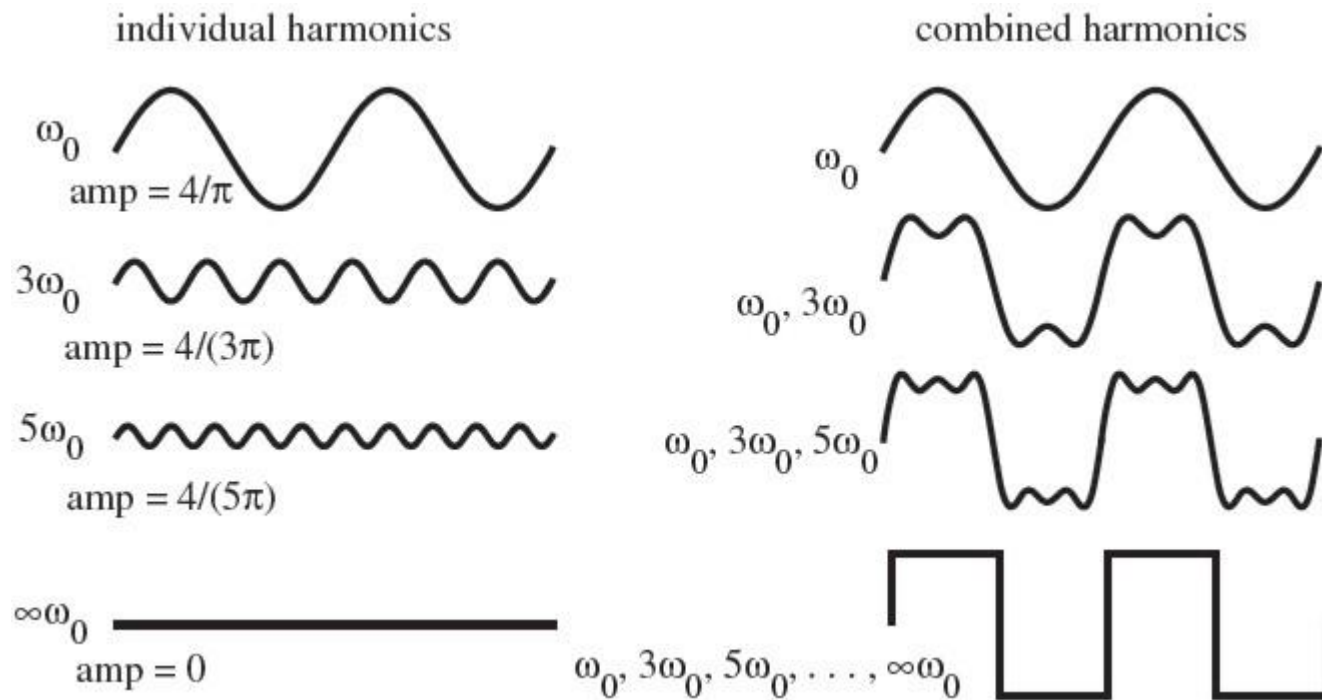


Problem?

-> Switching at 3\*f

# SNUB IT OUT

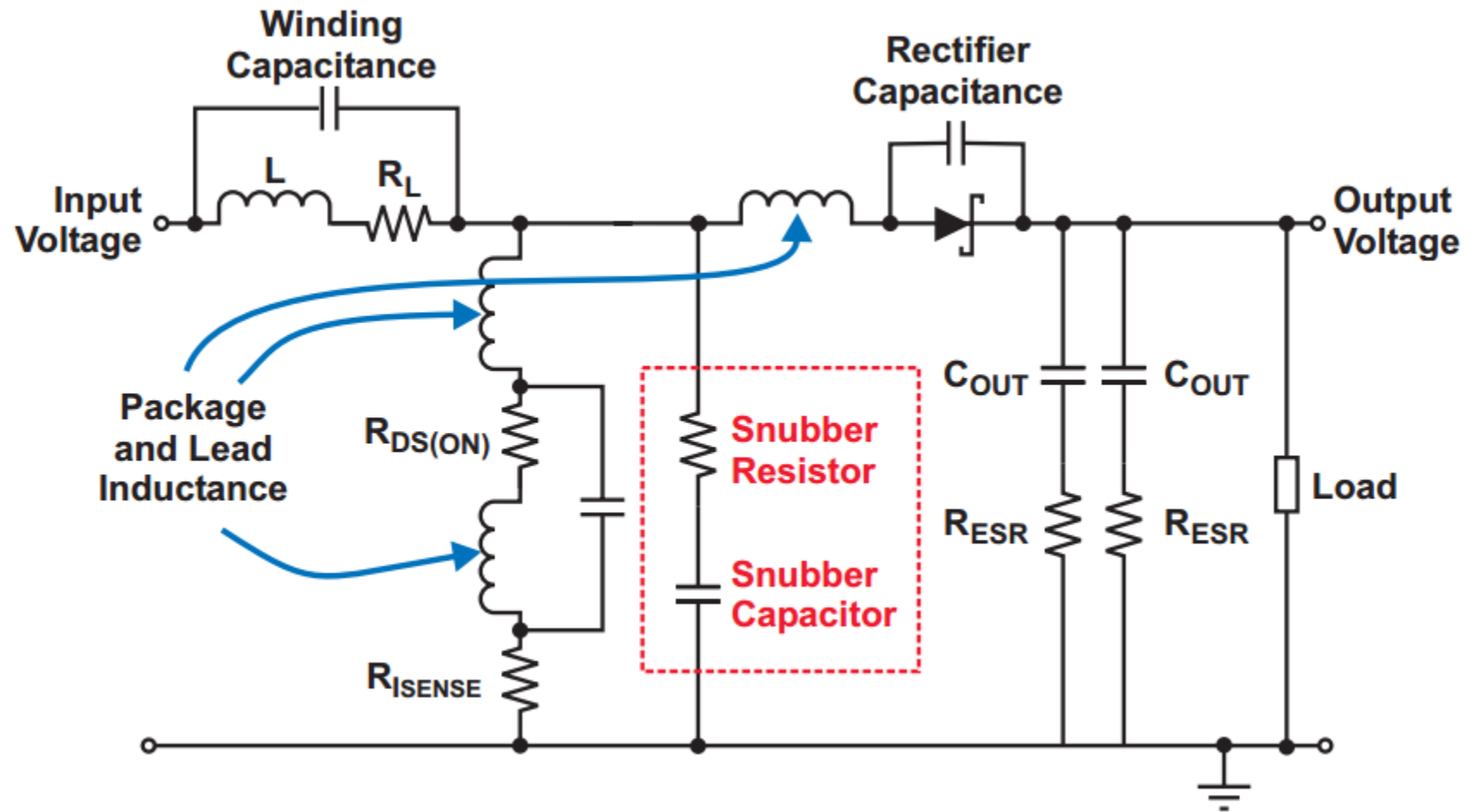

# IMPLEMENTATION

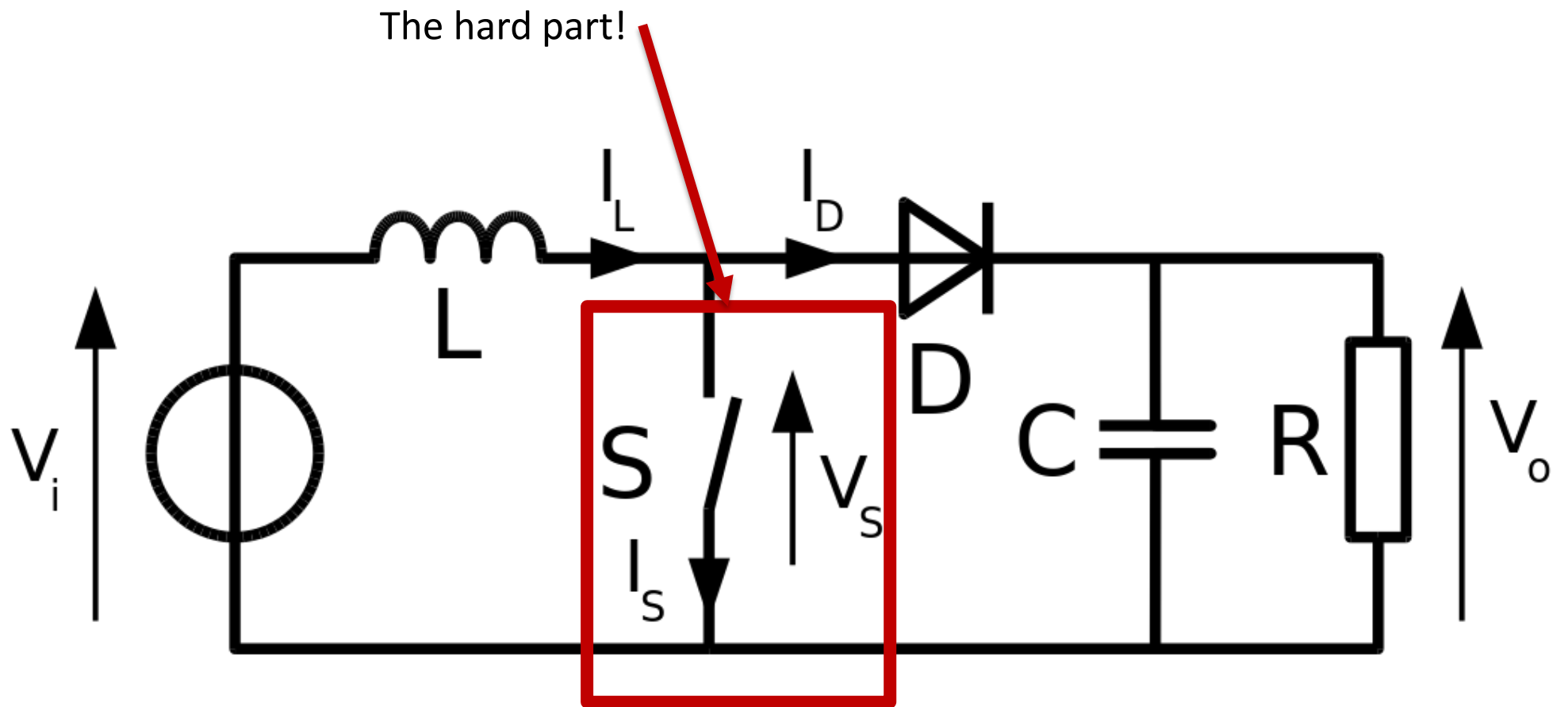

# LET SOMEONE ELSE HANDLE IT

## TYPICAL APPLICATION



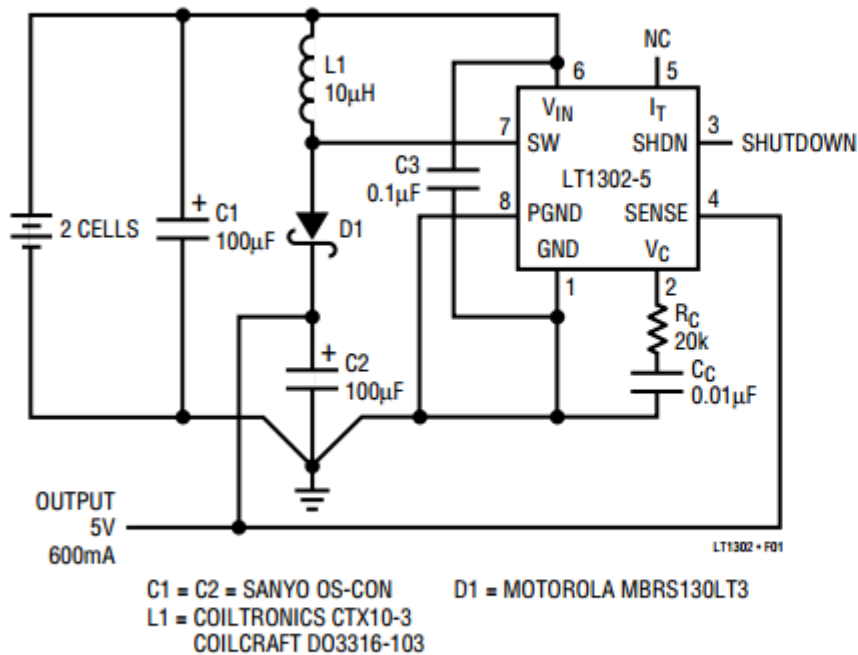


Figure 1. 2-Cell to 5V/600mA DC/DC Converter

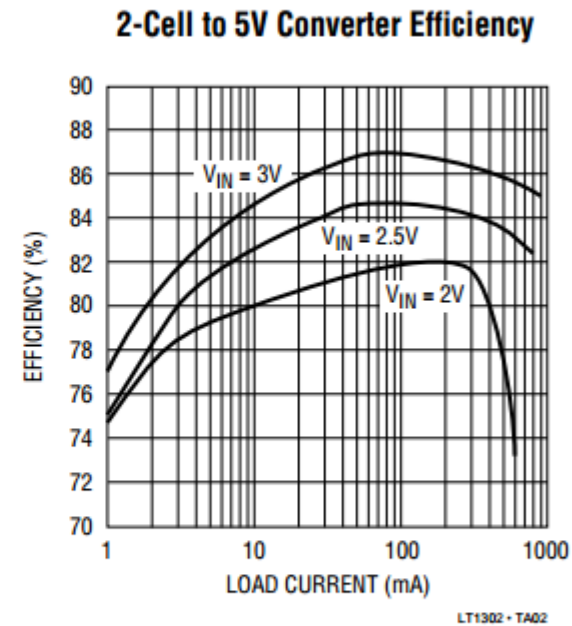


# WHAT'S INSIDE?

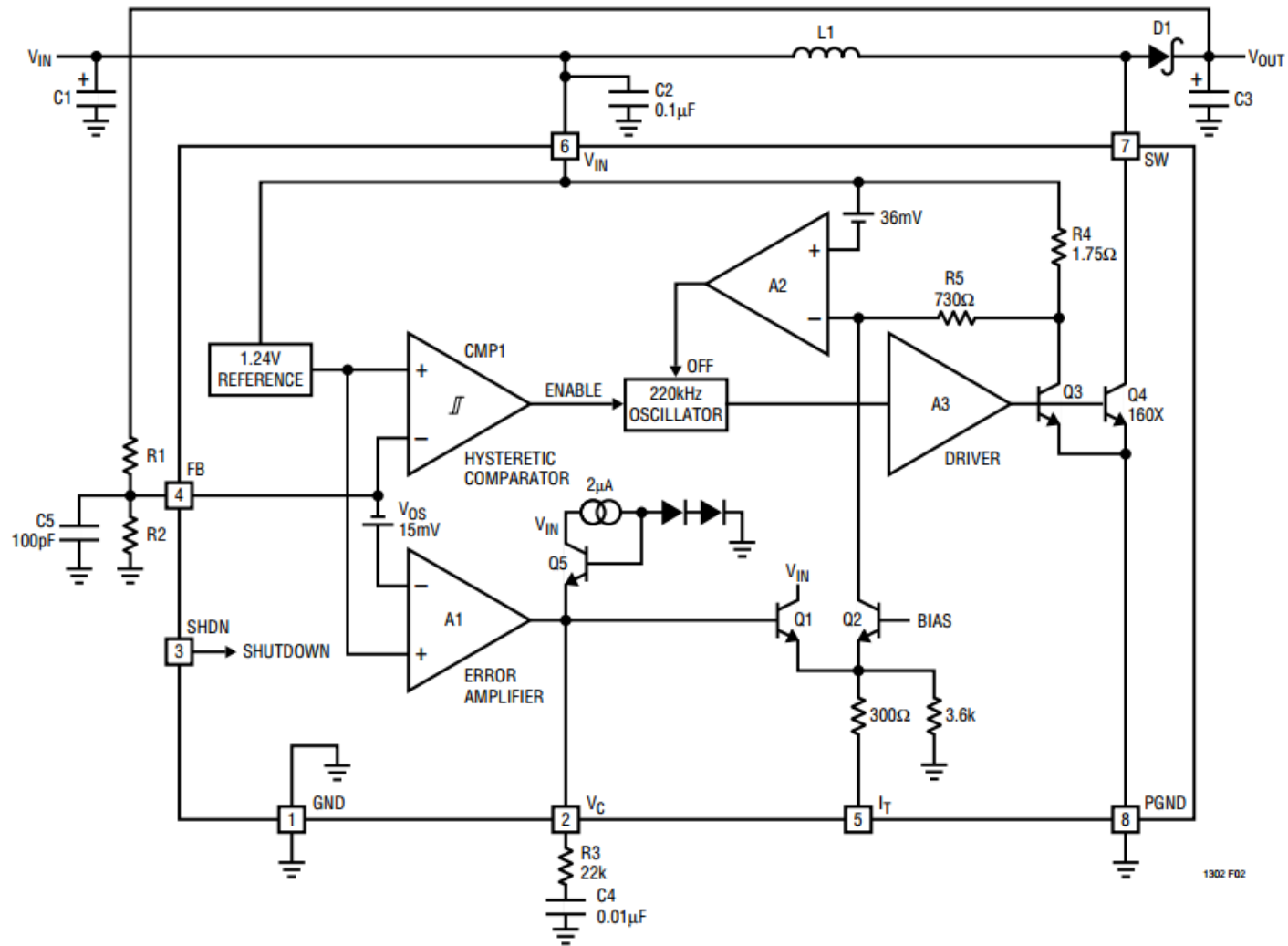





# SCHEMATIC

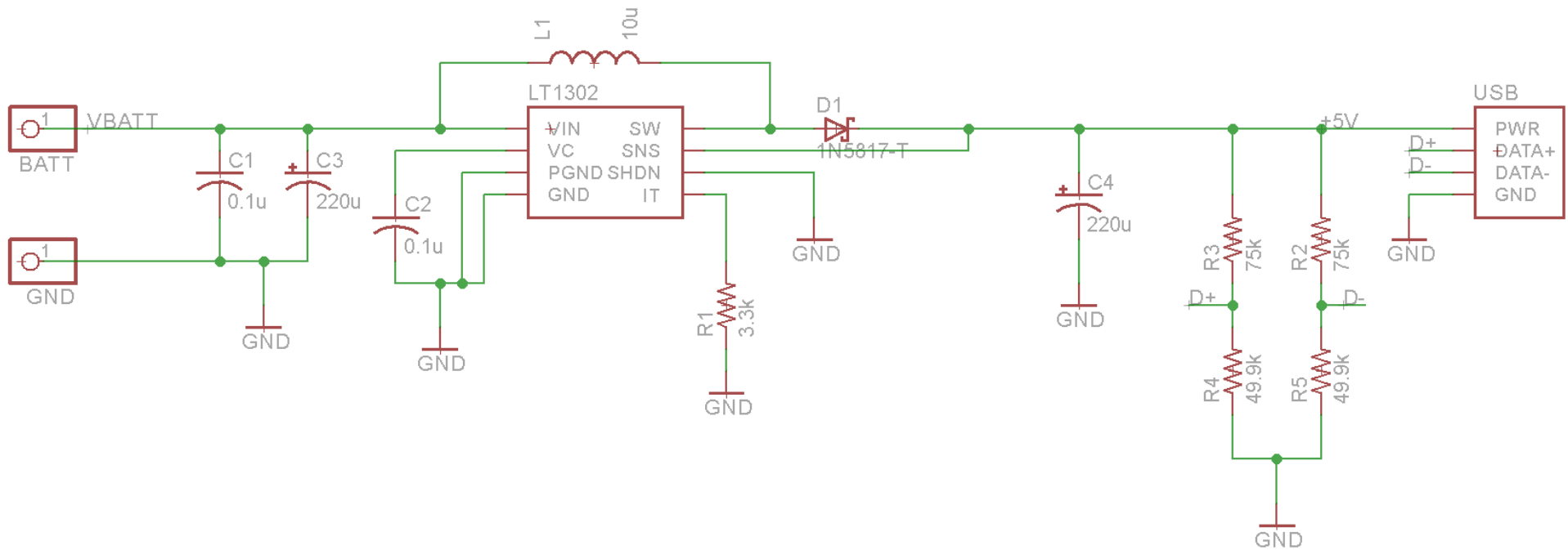

# PCB

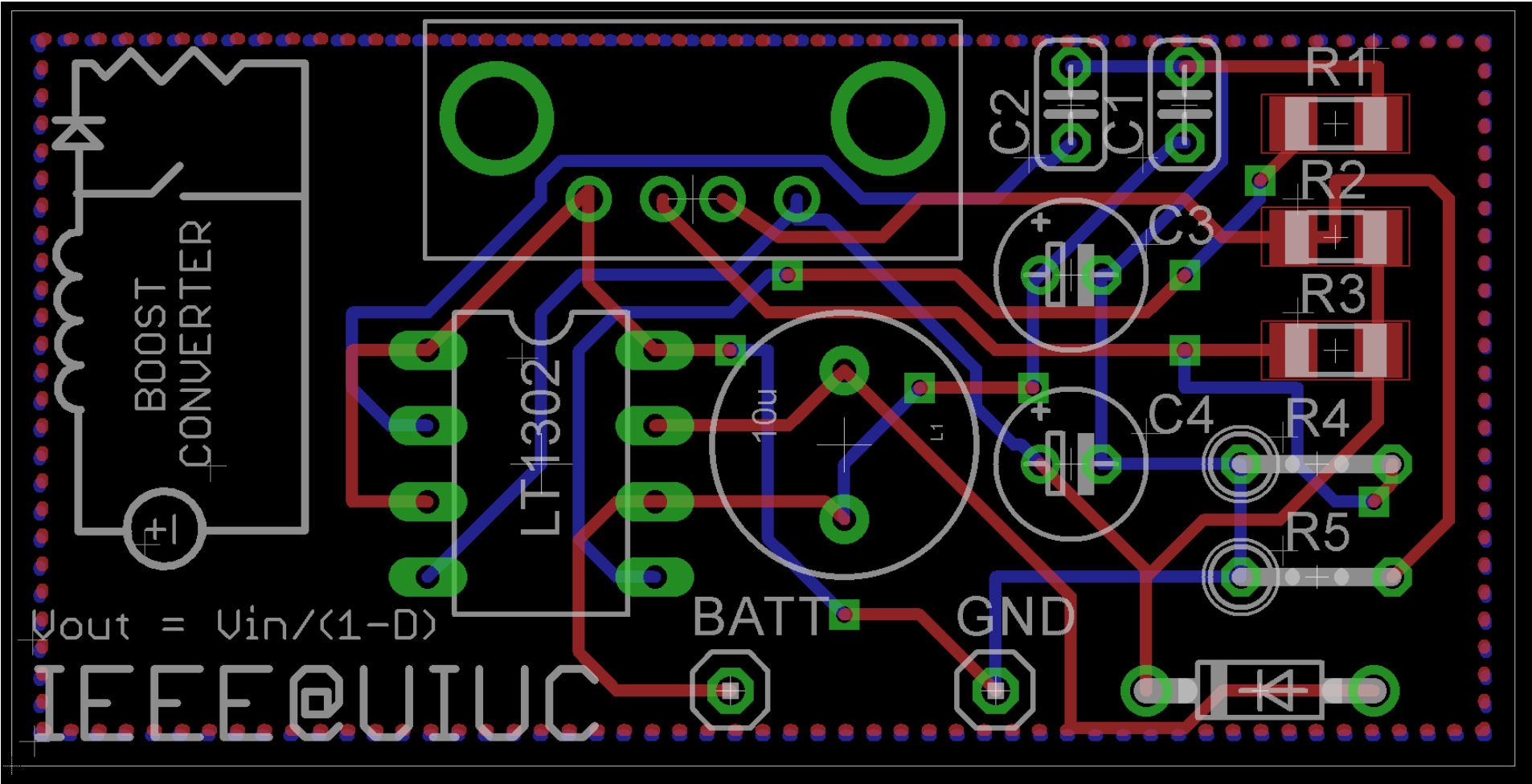

# BOARD

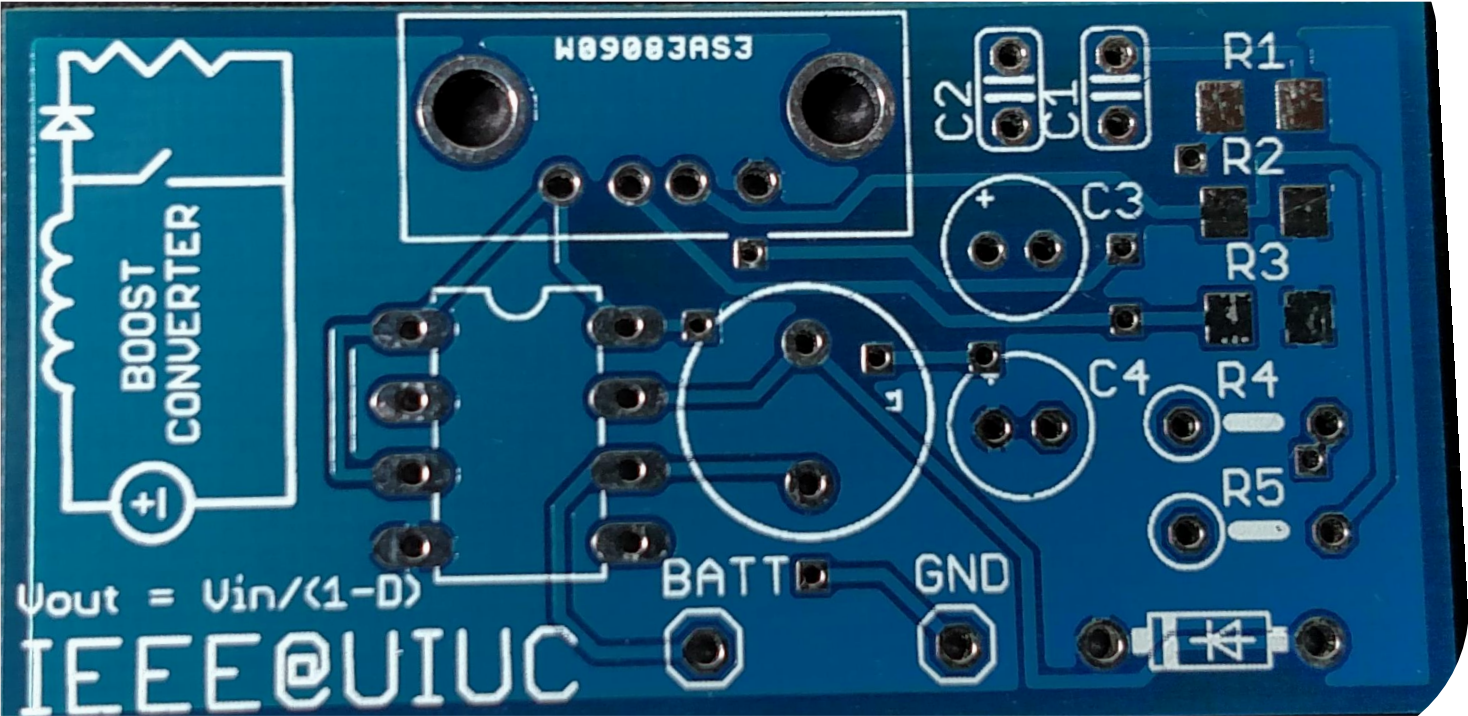

# CITATIONS

- “Under the Hood of a DC/DC Boost Converter” by Brian Lynch  
[http://www.ti.com/download/trng/docs/seminar/Topic\\_3\\_Lynch.pdf](http://www.ti.com/download/trng/docs/seminar/Topic_3_Lynch.pdf)
- “Boost Converter” – Wikipedia  
[https://en.wikipedia.org/wiki/Boost\\_converter](https://en.wikipedia.org/wiki/Boost_converter)
- LT1302 Datasheet  
<http://www.linear.com/product/LT1302>
- “MintyBoost Documentation” – Adafruit  
<https://learn.adafruit.com/minty-boost/>